

8.27 RLC parallel circuit **

A 1000 ohm resistor, a 500 picofarad capacitor, and a 2 millihenry inductor are connected in parallel. What is the impedance of this combination at a frequency of 10 kilocycles per second? At a frequency of 10 megacycles per second? What is the frequency at which the absolute value of the impedance is greatest?

解: 由并联关系可知 $\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$

$$Z_1 = R \quad Z_2 = i\omega L \quad Z_3 = \frac{1}{i\omega C}$$

$$\text{当 } \omega = 10 \text{ kHz 时 } |Z| = 20.0 \Omega$$


$$\text{当 } \omega = 10 \text{ MHz 时 } |Z| = 198 \Omega$$

$$\frac{1}{Z} = \frac{1}{R} + i(\omega C - \frac{1}{\omega L})$$

当 Z 最大时 $\frac{1}{Z}$ 最小 当 $\omega = 0$ 时 阻抗最大.

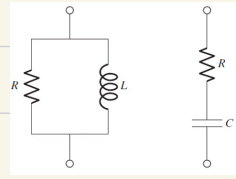8.30 Equal impedance? *

Do there exist values of R , L , and C for which the two circuits in Fig. 8.38 have the same impedance? (The resistor R has the same value in both.) Can you give a physical explanation why or why not?



解: $\frac{1}{Z_1} = \frac{1}{R} + \frac{1}{i\omega L}$ $\frac{1}{Z_1} = \frac{1}{R} - \frac{i}{\omega L}$ $\frac{1}{\frac{1}{R} - \frac{i}{\omega L}}$ $\frac{1}{(a-bi)} = \frac{a+bi}{a^2+b^2}$

$$Z_2 = R + i \frac{1}{\omega C}$$

令 $|Z_1| = |Z_2|$ 得 $\frac{1}{(\frac{1}{R})^2 + (\frac{1}{\omega L})^2} = R$ $\frac{\frac{\omega L}{R}}{(\frac{1}{R})^2 + (\frac{1}{\omega L})^2} = \frac{1}{\omega C}$ 无解. 不符合题意

即不存在 R, L, C 使得二者阻抗相等。

左图为电阻与电感并联, 总阻抗小于电阻阻抗。

右图为电阻与电容串联, 总阻抗大于电阻阻抗。

二者电阻相等, 则不存在 R, L, C 使得二者阻抗相等。

8.38 Two resistors and a capacitor **

The circuit in Fig. 8.42 has two equal resistors R and a capacitor C . The frequency of the emf source, $\mathcal{E}_0 \cos \omega t$, is chosen to be $\omega = 1/RC$.

- What is the total complex impedance of the circuit? Give it in terms of R only.
- If the total current through the circuit is written as $I_0 \cos(\omega t + \phi)$, what are I_0 and ϕ ?
- What is the average power dissipated in the circuit?

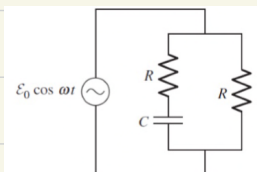


Figure 8.42.

解: (a). 由并联关系, $\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$

$$Z_1 = R + i \frac{1}{\omega C} = R + iR$$

$$Z_2 = R$$

$$\text{得 } Z = \frac{3}{5}R + i \frac{1}{5}R$$

$$(b). \hat{I}(t) = I_0 e^{i(\omega t + \phi)} \quad \hat{V} = \mathcal{E}_0 e^{i\omega t}$$

$$\hat{I}(t) = \frac{\hat{V}}{Z} = \frac{\sqrt{10}\mathcal{E}_0}{2R} e^{i(\omega t - \tan^{-1} \frac{1}{3})}$$

$$\text{则 } I_0 = \frac{\sqrt{10}\mathcal{E}_0}{2R} \quad \phi = -\tan^{-1} \frac{1}{3}$$

$$(c). \bar{P} = \frac{1}{2} \mathcal{E}_0 \frac{\sqrt{10}\mathcal{E}_0}{2R} \cdot \frac{3}{\sqrt{10}} \\ = \frac{3\mathcal{E}_0^2}{4R}$$